

Electric Circuits

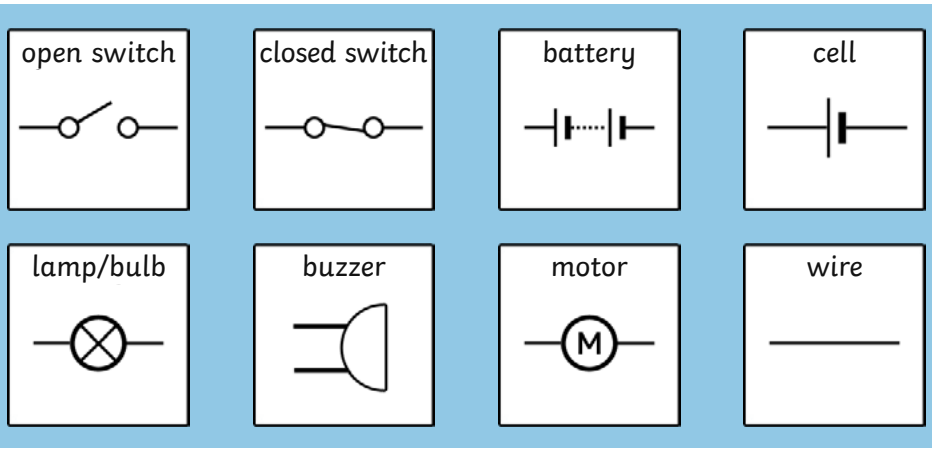Electricity flows in a circuit from the negative pole of a battery to its positive pole. The flow of electricity creates an electric current. There is a symbol to represent each component in an electrical circuit. Sometimes a lamp is called a bulb.



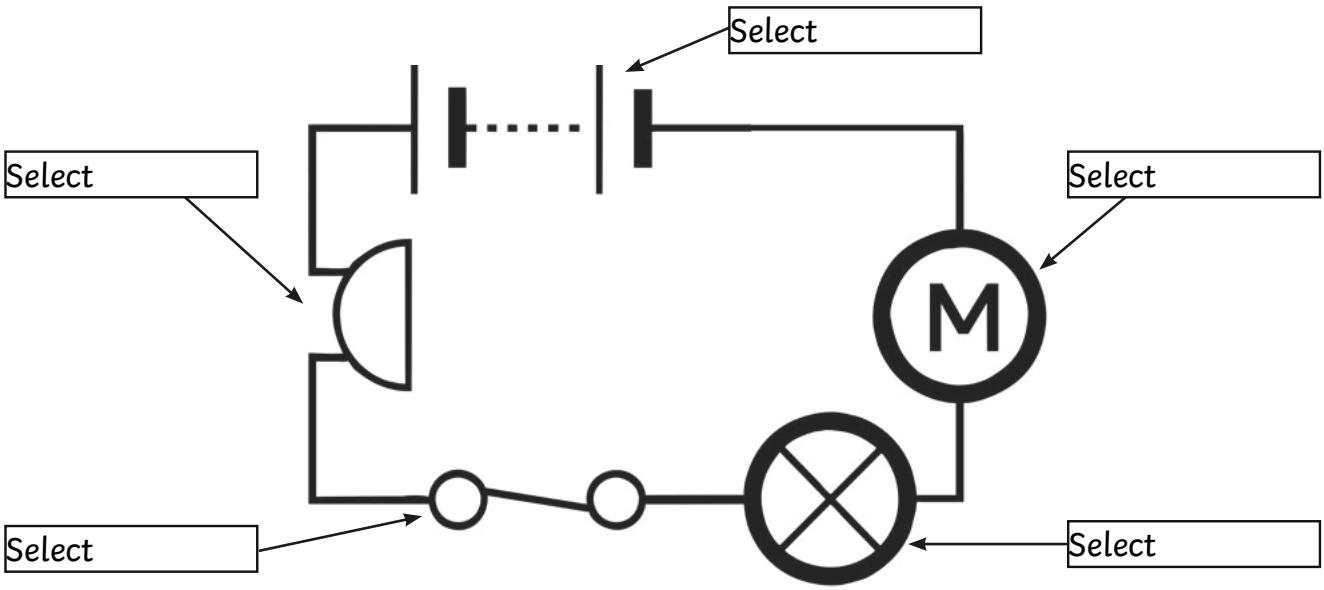Select the correct component to label the circuit below.



Complete the sentences about the circuit above.

The electric current leaves the _____ and passes through the _____. It then travels through the _____, next through the _____ and finally through the _____ before returning to the battery.

Click Here for Support with using Interactive PDFs